

Elektronika Memo

November 2018

1.3 A✓✓

1.6 A✓✓

QUESTION 11/VRAAG 11

11.1.1 (a) $V_1 = 24$ (V)✓ (1)

(b) $A_1 = 0$ (A)✓ (1)

11.1.2 <u>OPTION 1/OPSIE 1</u> $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \checkmark$ $= \frac{1}{8} + \frac{1}{8} \checkmark$ $R_p = 4 \Omega$ $R_T = R_s + R_p$ $= 8 + 4 \checkmark$ $= 12 \Omega \checkmark$	<u>OPTION 2/OPSIE 2</u> $R_p = \frac{\text{product / produk}}{\text{sum / som}} \checkmark$ $= \frac{(8)(8)}{8+8} \checkmark$ $= 4 \Omega$ $R_T = R_s + R_p$ $= 8 + 4 \checkmark$ $= 12 \Omega \checkmark$
---	--

(4)

11.1.3 <u>OPTION 1/OPSIE 1</u> V divides in a ratio 8 : 4 ✓ (series)/ V verdeel in 'n verhouding 8 : 4 (serie) $V_2 = \frac{8}{12} \times 24 \checkmark$ or/of $V_2 = \frac{2}{3} \times 24$ $= 16 V \checkmark$

<u>OPTION2 / OPSIE 2</u> POSITIVE MARKING FROM 11.1.2/POSITIEWE NASIEN VANAF 11.2.1 $V = IR$ $24 = I(12)$ $I = 2 A$ $V = IR \checkmark$ $= (2)(8) \checkmark$ $= 16 V \checkmark$

(3)

11.1.4 $A_2 = A_3 . \checkmark$ (1)

11.2.1 Resistance is directly proportional to the length of the conducting wire. ✓/
Weerstand is direk eweredig aan die lengte van die geleidingsdraad.

OR/OF

As the length of the wire increases, the resistance increases./*Soos die lengte van die geleidingsdraad toeneem, neem die weerstand toe* (1)

11.2.2 $1,35 \Omega \checkmark$ (Range/Variasiewyde: 1,3 Ω to/tot 1,4 Ω) (1)

[12]

Elektronika Memo

November 2017

1.10 D✓✓

(2)

QUESTION/VRAAG 11

11.1 Work done per unit charge by the source (battery) ✓✓

Die arbeid verrig per eenheidslading deur die bron (battery) ✓✓

(2)

$$11.2 \quad \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{1,5} + \frac{1}{1,5} \checkmark$$

$$= \frac{2}{3} + \frac{2}{3}$$

$$= \frac{4}{3}$$

$$\therefore R_p = \frac{3}{4} = 0,75 \Omega \checkmark$$

$$\begin{aligned} R_p &= \frac{R_1 \times R_2}{R_1 + R_2} \\ &= \frac{1,5 \times 1,5}{1,5 + 1,5} \checkmark \\ \therefore R_p &= 0,75 \Omega \checkmark \end{aligned}$$

(2)

11.3.1 1,5 A ✓

(1)

11.3.2

$$V_T = V_1 + V_2$$

$$9 = V_1 + 2V_1 \checkmark$$

$$9 = 3V_1 \checkmark$$

$$V_1 = 3V \checkmark$$

Accept/Aanvaar

$$V = IR \checkmark$$

$$V = 1,5(2) \checkmark$$

$$V = 3V \checkmark$$

(3)

11.4 • INCREASE✓/TOENEEM ✓

• If 1,5 Ω resistor is added, the resistance of the whole circuit decreases ✓
Indien 1,5 Ω resistor bygevoeg word, neem die totale weerstand van die stroombaan af. ✓

• Since $R \propto \frac{1}{I}$, if R decreases, ∴ V is constant and I of the circuit increases✓
Aangesien $R \propto \frac{1}{I}$, indien R afneem en V konstant bly, sal I van die stroombaan toeneem. ✓

(3)

[11]

Elektronika Memo

November 2016/1

1.10 B ✓✓

(2)

QUESTION 11/VRAAG 11

11.1.1

OPTION 1/OPSIE 1	OPTION 2/OPSIE 2
$\frac{1}{R_{\parallel}} = \frac{1}{R_1} + \frac{1}{R_2} \checkmark$ $= \frac{1}{6} + \frac{1}{3} \checkmark$ $\therefore R_{\parallel} = 2\Omega$ $\therefore R_{\text{total/totaal}} = 4 + 2\checkmark$ $= 6 \Omega \checkmark$	$R_{\parallel} = \frac{R_1 \times R_2}{R_1 + R_2} \checkmark$ $= \frac{6 \times 3}{6+3} \checkmark$ $= 2\Omega$ $\therefore R_{\text{total/totaal}} = 4 + 2\checkmark$ $= 6 \Omega \checkmark$

(4)

11.1.2

R _{parallel} : R _{series}	ACCEPT/ AANVAAR:
$2\Omega : 4\Omega \checkmark$ <p>∴ potential difference is also in ratio of Potensiaal verskil is ook in die verhouding 2: 4 or 1:2 ✓</p> $\therefore 12V \div 3 \text{ parts/dele} = 4V$ $\therefore V_{\text{series}} = 2 \times 4 = 8V \checkmark$	$R_{4\Omega} = \frac{V_2}{I_T} \checkmark$ $4 = \frac{V_2}{2} \checkmark$ $\therefore V_2 = 8V \checkmark$

(3)

Elektronika Memo

November 2016/2

<p>11.1.3 $R \propto \frac{1}{I}$ or in words: resistance is inversely proportional to current and \therefore ratio of resistors is $6 : 3 \checkmark$ $2 : 1$</p> <p>\therefore ratio of current is $1 : 2 \checkmark$ $A_2 : A_3$</p> $\therefore I_{A2} = \frac{2}{3} \times 1$ $\therefore I_{A2} = 0,67 \text{ A } \checkmark$ <p>$R \propto \frac{1}{I}$ in woorde: weerstand is omgekeerd eweredig aan stroom \therefore verhouding van resistors is $6 : 3 \checkmark$ $2 : 1$</p> <p>\therefore verhouding van stroom is $1 : 2 \checkmark$ $A_2 : A_3$</p> $\therefore I_{A2} = \frac{2}{3} \times 1$ $\therefore I_{A2} = 0,67 \text{ A } \checkmark$	<p>ACCEPT/AANVAAR:</p> $I = \frac{V}{R}$ $= \frac{12 - 8}{6}$ $= 0,67 \text{ A } \checkmark$	(3)
--	---	-----

11.1.4 $A_1 = 2 \text{ A}$
 $\therefore Q = I \Delta t \checkmark$
 $= 2 \times 120 \checkmark$
 $= 240 \text{ C } \checkmark$ (3)

11.2 Decrease \checkmark
Afneem (1)

- 11.3 **NEGATIVE MARKING FROM 11.2**
NEGATIEWE MERK VANAF 11.2
- If the 6Ω resistor is removed, the resistance of the whole circuit increases \checkmark
 - Since $R \propto \frac{1}{I} \checkmark$, if R increases, and V is constant \checkmark and I of the circuit decreases
 - Indien die 6Ω -resistor verwijder word, sal die totale weerstand van die stroombaan verhoog.
 - $R \propto \frac{1}{I} \checkmark$, so indien R verhoog en V bly konstant \checkmark , sal die stroom (I) verlaag. (3)
[17]

QUESTION 11/VRAAG 11

11.1.1 Current/Stroom.✓

(1)

11.1.2 The bulbs are identical and in series✓/the same current flows through each of the bulbs

Die gloeilampe is identies en in series/dieselde stroom vloei deur elk van die gloeilampe

OR/OF

The same amount of charge passes through each of them in any given time.

Dieselde aantal lading beweeg deur elk van hulle in enige gegewe tyd.

OR/OF

The potential difference across each of them is the same hence current is the same.

Die potensiaalverskil oor elk van hulle is dieselde en gevoglik is die stroom dieselde.

(1)

11.1.3 Decrease/Afneem ✓ (1)

11.2.1 Potential difference across a conductor is the energy per unit charge flowing through it. ✓✓

Die potensiaalverskil oor 'n geleier is die energie per eenheidslading wat deur dit vloei.

OR/OF

Work done per unit charge across the conductor. ✓✓

Arbeid verrig per eenheidslading oor die geleier.

(2)

<p>11.2.2</p> $\frac{1}{R_{\parallel}} = \frac{1}{R_1} + \frac{1}{R_2} \checkmark$ $= \frac{1}{2} + \frac{1}{6} \checkmark$ $\therefore R_{\parallel} = 1,5 \Omega \checkmark$	<p>OR/OF</p> $R_{\parallel} = \frac{R_1 R_2}{R_1 + R_2} \checkmark$ $\frac{2 \times 6}{2 + 6} \checkmark$ $\therefore R_{\parallel} = 1,5 \Omega \checkmark$
--	---

(3)

11.2.3 **POSITIVE MARKING FROM QUESTION 11.2.2**

POSITIEWE NASIEN VANAF VRAAG 11.2.2

OPTION 1/OPSIE 2

A series circuit acts as a potential divider./

'n Serieskakeling dien as 'n potensiaalverdeler

$$V_p = \frac{R_p}{R_{\text{tot}}} (V_{\text{tot}}) \checkmark$$

$$4 = \frac{1,5}{(1,5 + 4)} \times V_{\text{tot}} \checkmark$$

$$\therefore V_1 = V_{\text{tot}} = 14,67 \text{ V} \checkmark \checkmark$$

OPTION 2/OPSIE 2

$$V = IR \checkmark$$

$$4 = I(1,5) \checkmark$$

$$I = 2,667 \text{ A}$$

$$V_2 = IR = 2,667(4) \checkmark \\ = 10,67 \text{ V}$$

$$V_1 = V_{\text{tot}} = (4 + 10,67) \checkmark \\ = 14,67 \text{ V} \checkmark \checkmark$$

(4)

11.2.4 **POSITIVE MARKING FROM QUESTION 11.2.3**

POSITIEWE NASIEN VANAF VRAAG 11.2.3

$$V_2 = V_{\text{tot}} - V_{\parallel} \\ = (14,67 - 4) \checkmark \\ = 10,67 \text{ V} \checkmark \checkmark$$

OR/OF

$$V_2 = \frac{R_2}{R_{\text{tot}}} (V_{\text{tot}}) \\ = \frac{4}{(1,5 + 4)} \times 14,67 \checkmark \\ = 10,67 \text{ V} \checkmark \checkmark$$

(2)

[14]