

**Elektriese Stroombane Memo**  
**November 2018/1**



**QUESTION 12/VRAAG 12**

12.1

<p><b>OPTION 1/OPSIE 1</b></p> $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \quad \checkmark$ $\frac{1}{4,8} = \frac{1}{4R} + \frac{1}{6R} \quad \checkmark$ $R = 2 \Omega \quad \checkmark$	<p><b>OPTION 2/OPSIE 2</b></p> $R_p = \frac{R_1 R_2}{R_1 + R_2} \quad \checkmark$ $4,8 = \frac{4R \times 6R}{4R + 6R} \quad \checkmark$ $R = 2 \Omega \quad \checkmark$
--	---

(3)

12.2

<p><b>POSITIVE MARKING FROM QUESTION 12.1</b>  <b>POSITIEWE NASIEN VANAF VRAAG 12.1</b></p>	
<p><b>OPTION 1/OPSIE 1</b></p> $V_{4R} = IR_{4R}$ $= 1,8(4)(2) \quad \checkmark$ $= 14,4 \text{ V}$ $I_{6R} = \frac{V}{R_{6R}}$ $I_{6R} = \frac{14,4}{12} \quad \checkmark$ $= 1,2 \text{ A}$ $V_{2R} = IR \quad \checkmark$ $= 1,2(4) \quad \checkmark$ $= 4,8 \text{ V} \quad \checkmark$	<p><b>OPTION 2/OPSIE 2</b></p> $V_{4R} = IR_{4R}$ $= 1,8(4)(2) \quad \checkmark$ $= 14,4 \text{ V}$ $I_T = \frac{V}{R_T}$ $I_T = \frac{14,4}{4,8}$ $= 3 \text{ A}$ $I_{2R} = 3 - 1,8 \quad \checkmark$ $= 1,2 \text{ A}$ $V_{2R} = IR \quad \checkmark$ $= 1,2(4) \quad \checkmark$ $= 4,8 \text{ V} \quad \checkmark$
<p><b>OPTION 3/OPSIE 3</b></p> $R_1 : R_2$ $4 : 6$ $I_1 : I_2$ $6 : 4$ $\frac{6}{10} \times I = 1,8 \text{ A} \quad \checkmark$ $I_T = 3 \text{ A}$ $I_{2R} = 3 - 1,8 \quad \checkmark$ $= 1,2 \text{ A}$ $V_{2R} = IR \quad \checkmark$ $= 1,2(4) \quad \checkmark$ $= 4,8 \text{ V} \quad \checkmark$	<p><b>OPTION 4/OPSIE 4</b></p> $V_{4R} = IR_{4R}$ $= 1,8(4)(2) \quad \checkmark$ $= 14,4 \text{ V}$ $R : 2R : 3R$ $1 : 2 : 3$ $V_R : V_{2R} : V_{3R}$ $1 : 2 : 3$ $V_{2R} = \frac{2}{\sqrt{6}} \times 14,4 \quad \checkmark$ $= 4,8 \text{ V} \quad \checkmark$

(5)

Elektriese Stroombane Memo

November 2018/2


12.3

<b>POSITIVE MARKING FROM QUESTION 12.1 AND 12.2</b> <b>POSITIEWE NASIEN VANAF VRAAG 12.1 EN 12.2</b>		
<b>OPTION 1/OPSIE 1</b> $W = I^2 R \Delta t \checkmark$ $= 1,8^2(8)(120) \checkmark$ $= 1036,8 \text{ J} \checkmark$	<b>OPTION 2/OPSIE 2</b> $W = VI\Delta t \checkmark$ $= (14,4)(1,8)(120) \checkmark$ $= 3110,4 \text{ J} \checkmark$	<b>OPTION 3/OPSIE 3</b> $W = \frac{V^2 \Delta t}{R} \checkmark$ $W = \frac{(14,4)^2 (120)}{8} \checkmark$ $W = 3110,4 \text{ J} \checkmark$

(3)

12.4 Decrease/Neem af  $\checkmark$

(1)

12.5  The ammeter has such a low resistance  $\checkmark$   
 It short circuits the parallel part and all current flows through the ammeter.  $\checkmark$   
**OR**  
 The ammeter short circuits the resistors  $\checkmark$   
 No current flows through resistor 2R  $\checkmark$

*Die ammeter het so 'n lae weerstand*  
*Dit kortsluit die parallelgedeelte en al die stroom vloei deur die ammeter.*

**OF**  
 Die ammeter kortsluit die resistors  
 Daar vloei geen stroom deur resistor 2R nie

(2)  
**[14]**

Elektriese Stroombane Memo

November 2017/1

1.10 B ✓✓

(2)

**QUESTION/VRAAG 10**

10.1.1 Power is the rate at which work is done/energy is transferred. ✓✓

*Drywing is die tempo waarteen arbeid verrig /energie oorgedra word ✓✓*

(2)

10.1.2

OPTION 1/OPSIE 1	OPTION 2/OPSIE 2
$\frac{1}{R_{//}} = \frac{1}{R_1} + \frac{1}{R_2}$ $\frac{1}{R_{//}} = \frac{1}{6} + \frac{1}{15} \checkmark$ $R_{//} = 4,29 \Omega \checkmark$	$R_{//} = \frac{R_1 \times R_2}{R_1 + R_2}$ $R_{//} = \frac{6 \times 15}{6 + 15} \checkmark$ $R_{//} = 4,29 \Omega \checkmark$

(2)

10.1.3 **POSITIVE MARKING FROM QUESTION 10.1.2**

**POSITIEWE NASIEN VANAF VRAAG 10.1.2**

$$P = \frac{V^2}{R} \checkmark$$

$$50 = \frac{V^2}{4,29} \checkmark$$

$$V = 14,65 \text{ V} \checkmark$$

(3)

10.1.4 **POSITIVE MARKING FROM QUESTION 10.1.2 and 10.1.3**

**POSITIEWE NASIEN VANAF VRAAG 10.1.2 en 10.1.3**

OPTION 1/OPSIE 1	OPTION 2/OPSIE 2
$R = \frac{V}{I} \checkmark$ $4,29 = \frac{14,65}{I} \checkmark$ $I = 3,41 \text{ A} \checkmark$	$P = VI \checkmark$ $50 = (14,65)I \checkmark$ $I = 3,41 \text{ A} \checkmark$
OPTION 3/OPSIE 3	OPTION 4/OPSIE 4
$P = I^2R \checkmark$ $50 = I^2(4,29) \checkmark$ $I = 3,41 \text{ A} \checkmark$	$V = IR \checkmark$ $14,65 = I(6)$ $I = 2,44 \text{ A}$ $V = IR$ $14,65 = I(15)$ $I = 0,98 \text{ A}$ $2,44 + 0,98 \checkmark = 3,42 \text{ A} \checkmark$

(3)

## Elektriese Stroombane Memo

November 2017/2

10.1.5 Decreases ✓

*Neem af ✓*

(1)



10.1.6 The total resistance increases ✓

The current in the circuit decreases ✓

The resistance of R is constant, ✓ then the potential difference across R decreases.

*Totale weerstand neem toe ✓*

*Die stroom in die stroombaan neem af ✓*

*Die weerstand van R is konstant ✓ so die potensiaalverskil oor resistor R sal afneem*

(3)

10.2.1

$$P = \frac{W}{\Delta t} \checkmark$$

$$2\,000 \checkmark = \frac{W}{18\,000} \checkmark$$

$$W = 3,6 \times 10^7 \text{ J } \checkmark$$

(4)

10.2.2 Cost = price x unit kWh / *Koste = prys x eenheid kWh*

$$\text{Cost} = 80(2)(5)(30) \checkmark$$

$$\text{Cost} = 24\,000 \text{ cents} = \text{R}240 \checkmark$$

(answer can be given in rand or cents)

*(antwoord kan in rand of sent gegee word)*

(2)

**[20]**

Elektriese Stroombane Memo

November 2016

1.3 C ✓✓ (2)

1.6 C ✓✓ (2)

9.1 The potential difference (voltage) across a conductor is directly proportional to the current ✓ in the conductor at constant temperature. ✓

*Die potensiaalverskil oor 'n geleier is direk eweredig aan die stroom in die geleier by konstante temperatuur.*

**OF/OR**

Ratio of potential difference to current is constant ✓ at constant temperature. ✓

*Die verhouding van die potensiaalverskil tot stroom is konstant by konstante temperatuur.*

(2)

9.2 **Option/Opsie 1**

$$R_p = \frac{(R_A \times R_B)}{(R_A + R_B)} \checkmark$$

$$2 \checkmark = \frac{(6 R_B) \checkmark}{(6 + R_B) \checkmark}$$

$$\begin{aligned} 2(6 + R_B) &= 6R_B \\ 12 + 2R_B &= 6R_B \\ R_B &= 3 \Omega \checkmark \end{aligned}$$

**Option/Opsie 2**

$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{R_A} + \frac{1}{R_B} \checkmark \\ \frac{1}{2} \checkmark &= \frac{1}{6} \checkmark + \frac{1}{R_B} \checkmark \\ \frac{1}{R_B} &= \frac{1}{2} - \frac{1}{6} \\ \frac{1}{R_B} &= \frac{2}{6} \end{aligned}$$

$$R_B = 3 \Omega \checkmark$$

(5)

9.3  $R_T = R_P + R_S \checkmark$   
 $= 2 \checkmark + 6 \checkmark$   
 $= 8 \Omega \checkmark$

$$I = \frac{V}{R} \checkmark = \frac{24}{8} \checkmark = 3A \checkmark$$

(7)

9.4 **Option/Opsie 1**

$$\begin{aligned} V_P &= IR_p \checkmark \\ &= 3 \checkmark \times 2 \checkmark \\ &= 6 V \checkmark \end{aligned}$$

$$V_p = V_A \checkmark = V_B$$

$$V_A = 6 V \checkmark \checkmark \text{ (2 or 0 marks/punte)}$$

**Option/Opsie 2**

$$\begin{aligned} V_C &= IR_6 \checkmark \\ &= 3 \checkmark \times 6 \checkmark \\ &= 18 V \checkmark \end{aligned}$$

$$V_T = V_p + V_C \checkmark$$

$$24 = V_p + 18$$

$$V_p = 6 V \checkmark \checkmark \text{ (2 or 0 marks/punte)}$$

(7)

[21]

1.9 A ✓✓

1.10 C ✓✓

**QUESTION/VRAAG 13**

13.1 13.1.1  $P = I^2 R$  ✓  
 $0,5 = I^2 8$  ✓  
 $I = 0,25 \text{ A}$  ✓

$$\frac{1}{R_p} = \frac{1}{r_1} + \frac{1}{r_2} \quad \checkmark = \frac{1}{6} + \frac{1}{(6+6)} \quad \checkmark = \frac{3}{12} \quad \therefore R_p = 4 \Omega$$

$$R_T = 8 + 4 \quad \checkmark = 12 \Omega$$

$$V_T = I R_T = (0,25)(12) = 3V \quad \checkmark \quad (8)$$

13.1.2  $V_p = I R \quad \checkmark = (0,25)(4) \quad \checkmark = 1V$   
 $I = \frac{V_p}{R} = \frac{1}{6} \quad \checkmark = 0,17 \text{ A} \quad \checkmark \quad (4)$

13.2 13.2.1  $P = \frac{V^2}{R} \quad \checkmark$   
 $750 \checkmark = \frac{240^2}{R} \quad \checkmark$   
 $R = 76,80 \Omega \quad \checkmark$

OR/OF

$$\checkmark \begin{cases} P = VI \\ 750 \checkmark = 240 I \quad \checkmark \\ I = 3,13 \text{ A} \\ \\ R = \frac{V}{I} \\ \\ = \frac{240}{3,13} \\ = 76,80 \Omega \quad \checkmark \end{cases} \quad (4)$$

13.2.2  $E = P \times t = 750 \times 6 \quad \checkmark = 4\,500 \text{ Wh} = 4,5 \text{ kWh}$

Cost/Koste =  $4,5 \times 1,14 \quad \checkmark = R\,5,13 \quad \checkmark$

OR/OF

Cost/Koste =  $(0,75)(6) \quad \checkmark (1,14) \quad \checkmark = R5,13 \quad \checkmark \quad (3)$



**QUESTION 11/VRAAG 11**

- 11.1 The potential difference across a conductor is directly proportional to the current in the conductor ✓ at constant temperature. ✓

*Die potensiaalverskil oor 'n geleier is direk eweredig aan die stroom in die geleier by konstante temperatuur.*

OR/OF

Provided temperature and other physical conditions are constant ✓, the potential difference across a conductor is directly proportional to the current ✓.

*Mits die temperatuur en ander fisiese toestande konstant is, is die potensiaalverskil oor 'n geleier direk eweredig aan die stroom.*

(2)

- 11.2 **OPTION 1/OPSIE 1**

$$\begin{aligned} V_1 &= IR_{6\Omega} \checkmark \\ &= 0,6(6) \checkmark \\ &= 3,6 \text{ V} \end{aligned}$$

$$I_{4\Omega} = \frac{3,6}{4} \checkmark$$

$$\therefore I_{4\Omega} = 0,9 \text{ A} \checkmark$$

**OPTION 2/OPSIE 2**

$$V = IR \checkmark$$

$$(0,6)(6) = I_{4\Omega}(4) \checkmark$$

$$\begin{aligned} I_{4\Omega} &= \frac{(0,6)(6)}{4} \checkmark \\ &= 0,9 \text{ A} \checkmark \end{aligned}$$

(4)

- 11.3 **POSITIVE MARKING FROM QUESTION 11.2.1**  
**POSITIEWE NASIEN VANAF VRAAG 11.2.1**

$$\begin{aligned} I_{\text{tot}} &= I_{6\Omega} + I_{4\Omega} \\ &= (0,6 + 0,9) \checkmark \end{aligned}$$

$$I_{\text{tot}} = 1,5 \text{ A} \checkmark$$

(2)

- 11.4 **POSITIVE MARKING FROM QUESTION 11.2.1 AND QUESTION 11.2.2**  
**POSITIEWE NASIEN VANAF VRAAG 11.2.1 EN VRAAG 11.2.2**

$$\begin{aligned} V_X &= V_{\text{tot}} - V_1 \\ &= (6 - 3,6) \checkmark \\ &= 2,4 \text{ V} \end{aligned}$$

$$V = IR \checkmark$$

$$X = \frac{2,4}{1,5}$$

$$= 1,6 \Omega \checkmark$$

(3)

**Elektriese Stroombane Memo**

**November 2014/2**

- 11.5 Energy/Energie  $W = I^2 R \Delta t$  ✓  
For the same time interval  $I^2 R \Delta t$  will be greater for the  $4\Omega$  resistor than for the  $6\Omega$  resistor. ✓  
Vir dieselfde tydinterval sal  $I^2 R \Delta t$  groter wees vir die  $4\Omega$ -resistor as vir die  $6\Omega$ -resistor.

OR/OF

Energy/Energie  $W = \frac{V^2}{R} \Delta t$  ✓

For the same potential difference and time  $\frac{V^2}{R} \Delta t$  is greater for the smaller resistance than for the larger resistance. ✓

Vir dieselfde potensiaalverskil en tyd is  $\frac{V^2}{R} \Delta t$  groter vir die kleiner weerstand as vir die groter weerstand.

(3)  
[14]

**Elektriese Stroombane Memo**

**November 2013**

2.8 C

(2)

2.10 B

(2)

**QUESTION/VRAAG 11**

11.1	11.1.1	$3V \checkmark$	(1)	
	11.1.2	$I = V/R \checkmark = 3/5 \checkmark = 0,6 A \checkmark$	(3)	
	11.1.3	$I = V/R = 3 \checkmark / 7 \checkmark = 0,43 A$ $V_2 = IR \checkmark = 0,43 \times 4 \checkmark = 1,72 V \checkmark$ (accept/aanvaar 1,71 V)	(5)	
11.2	11.2.1	$P = \frac{V^2}{R} \checkmark$ OR/OF $P = VI$ $2600 \checkmark = \frac{220^2 \checkmark}{R}$ $2600 = 220 I \checkmark$ $R = 18,62 \Omega \checkmark$ $I = 11,82 A$ $R = V/I$ $= 220/11,82 \checkmark$ $= 18,62 \Omega \checkmark$	<div style="border: 1px solid black; padding: 5px; display: inline-block;">                     both equations/                      beide vergelykings  <math>\checkmark</math> </div>	(4)
	11.2.2	$Cost = (2,6 \times 3,5) \checkmark \times 1,04 \checkmark = R9,46 \checkmark$ OR/OF $E = Pt = 2,6 kW \times 3,5 h \checkmark = 9,1 kWh$ $Cost = 9,1 kWh \times R1,04 \checkmark = R9,46 \checkmark$	(3)	

**[16]**

## Elektriese Stroombane Memo

### Modelvraestel 2013

1.10 B ✓✓ (2)

#### QUESTION 12/VRAAG 12

12.1 Resistance = gradient of graph

12.1.1 *Weerstand = helling van grafiek*

$$= \frac{4 - 0}{25 \times 10^{-3} - 0}$$
$$= 160 \, \Omega$$

(3)

12.1.2 Graph at  $T_1$  / *Grafiek by  $T_1$*

Steeper/larger gradient / *Steiler helling*

$\therefore R$  is greater /  *$R$  is groter*

$\therefore$  Temperature is higher / *Temperatuur is hoër*

(3)

12.1.3  $V$  is directly proportional to  $I$  at each of the temperatures  $T_1$  and  $T_2$ .

*$V$  is direk eweredig aan  $I$  by elk van die temperature  $T_1$  en  $T_2$*

(1)

12.1.4  $P = VI$

$$= (2,5)(25 \times 10^{-3})$$

$$= 0,0625 \text{ W}$$

(3)

12.2

12.2.1 Both switches open: / *Beide skakelaars oop:*

$$R = 6 \, \Omega + 1 \, \Omega + 2 \, \Omega = 9 \, \Omega$$

$$R = \frac{V}{I}$$

$$9 = \frac{4,5}{I}$$

$$\therefore I = 0,5 \text{ A}$$

(4)

12.2.2 Both switches closed: / *Beide skakelaars gesluit:*

$$V_{6\Omega} = IR = (0,5)(6) = 3 \text{ V}$$

$$V_{2\Omega} = 4,5 - 3 = 1,5 \text{ V}$$

$$I_{2\Omega} = \frac{V}{R} = \frac{1,5}{2} = 0,75 \text{ A}$$

$$I_R = 0,75 - 0,5 = 0,25 \text{ A}$$

$$R = \frac{V}{I} = \frac{3}{0,25} = 12 \, \Omega$$

(6)

[20]